

**2022/23**  
**EE101 Laboratory Book**  
**Department of Electronic Engineering**

**Lab 2 : Resistance, Current and  
Voltage**  
*Handout and Answer Sheet*



Name :

Student ID :

## EQUIPMENT

A voltage source, voltmeters, ammeters, a laboratory lead kit. Pick three different resistors from the available resistors.

## OBJECTIVE

The objectives of this laboratory are for the student to calculate, implement and measure resistance, current and voltage. In doing so the student will for the first time gain experience using the test and measuring equipment provided for the laboratory.

## INFORMATION

1. Always use the measured value of resistance for all calculations.
2. Always adjust the power supply voltage with the circuit connected.
3. When measuring voltage, the voltmeter must be connected across the circuit.
4. When measuring current, you must break the circuit and the current meter must be inserted into the circuit (in series).
5. Remember the resistor colour-code!

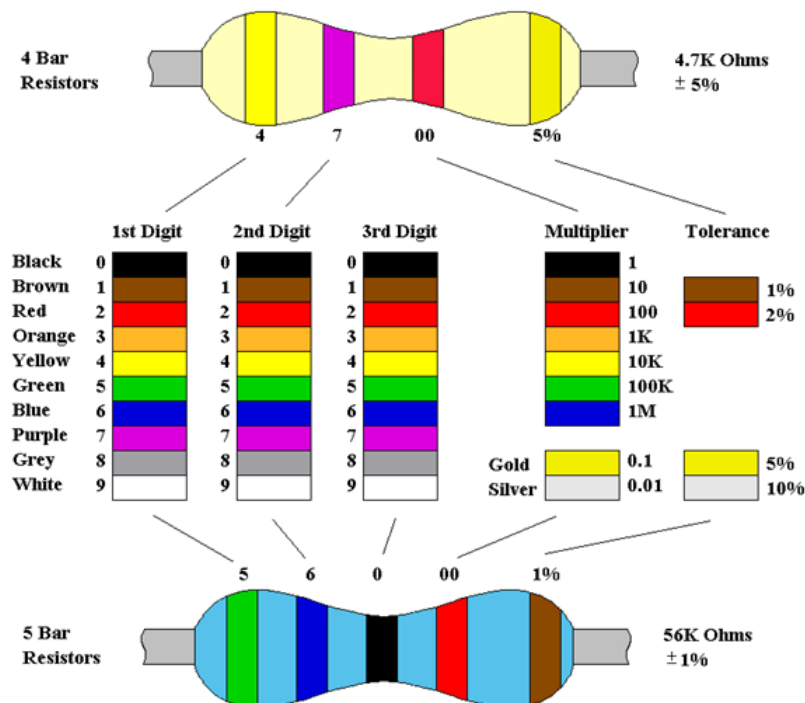


Figure 1: Resistance and related color codes

## PROCEDURE

### Part 1: Ohm's Law

You need to calculate the value of all the three resistors supplied using their color-code and fill in Table 1 accordingly. Ensure, the values of the resistors are high enough so that  $R$  gets very hot!! When reading resistors there is a figure for tolerance (the percentage error that this device is allowed to have). You can get the max and the min resistance values by taking the nominal "official" value and adding/subtracting the tolerance percentage.

Table 1: Answers for Part 1

	Resistor Colour-Code	Colour-Coded Resistance	Colour-Coded Tolerance	Max Coded Resistance	Min Coded Resistance	Measured Resistance	Is the resistor within Tolerance
$R_1$							
$R_2$							
$R_3$							

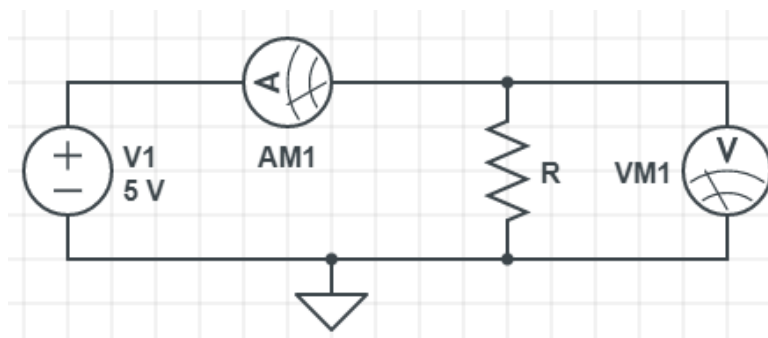


Figure 2

You may measure the resistance by constructing a circuit with a supplied voltage of 5 Volt, a voltmeter and an ammeter. The circuit you need is shown below (Fig. 2). Using ohm's law, calculate the real resistance (measured resistance) of the device and fill in Table 1. You must use an ammeter and a voltmeter to take your measurements. *DO NOT USE AN OHMMETER.*

### Part 2: Resistors in Series

#### Part 2.1

- On your bread-board connect the circuit shown in Fig. 3.
- Calculate and then measure the total resistance. You may measure the individual resistances using the color codes. You may measure the total resistance  $R_{Total}$  using a multi-meter.

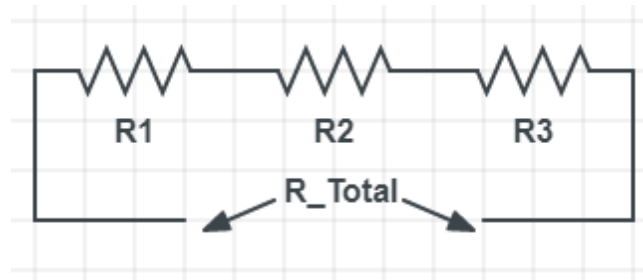


Figure 3

Table 2: Answers for Part 2.1

$R_1$	
$R_2$	
$R_3$	
Calculated $R_{Total}$	
Measured $R_{Total}$	

- Show your calculation.

## Part 2.2

- Connect the circuit in Fig. 4. Note that this circuit is the same as in Fig. 3, except that there is now a DC supply voltage connected. Set the voltage source to 5.0 volts. Break the circuit between the **POSITIVE side of the battery and resistor  $R_1$** . Insert the ammeter and measure and record the current flow through this point. Now do the same for the points between the other resistors and the **resistor  $R_3$  and the negative side of the battery**. Record the currents in Table 5.
- What conclusions can be made from these results?

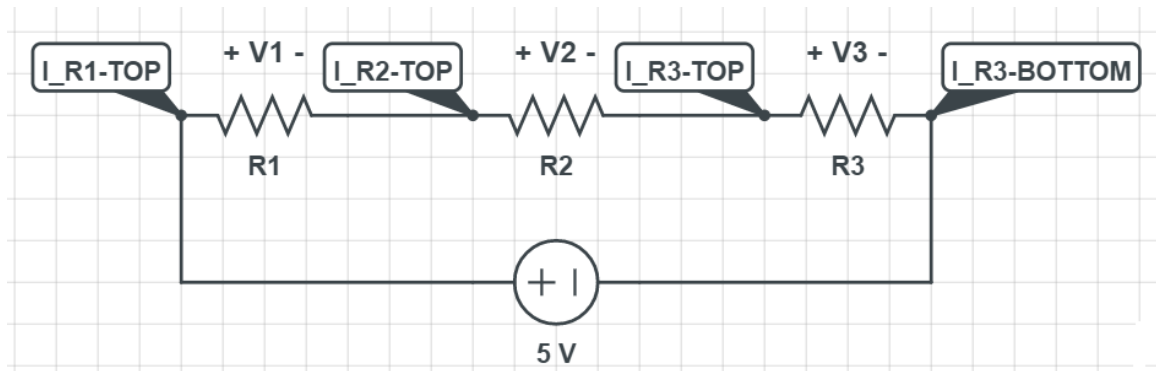


Figure 4

Table 3: Answers for Part 2.2

$I_{R1-TOP}$	
$I_{R2-TOP}$	
$I_{R3-TOP}$	
$I_{R3-BOTTOM}$	

**Part 2.3**

- Connect the circuit of Fig. 4. Set the DC supply voltage to 5.0 volts. Measure the voltage drop across each resistor. Record in Table 4. Add the voltage drops together and record.

Table 4: Answers for Part 2.3

$V_1$	
$V_2$	
$V_3$	
Total of Voltage Drops	

- What conclusions can be made from these results?

### Part 3: Resistors in Parallel

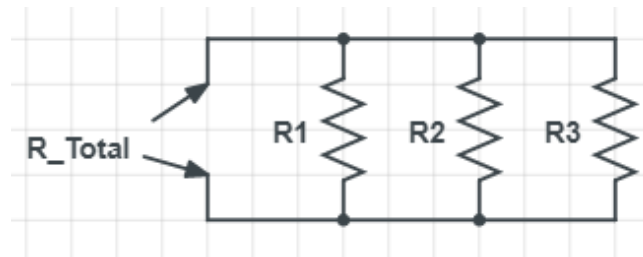


Figure 5

#### Part 3.1

- On your bread-board connect the circuit shown in Fig. 5. Calculate and then measure the total resistance. Show your calculation. For the measurement you may use the same technique as done in Part 1. You may measure the individual resistances using the color codes. You may measure the total resistance  $R_{Total}$  using a multi-meter.

Table 5: Answers for Part 3.1

Calculated $R_{Total}$	
Measured $R_{Total}$	

- Show your calculation.

#### Part 3.2

- Connect the circuit in Fig. 6. Make sure that the source voltage is properly set to 5 volts with the circuit connected. Measure the current through each resistor and the total current. Record in Table 6.

- Add the measured currents through  $R_1$ ,  $R_2$ , and  $R_3$  together and compare with the measured total current. Record the sum of measured currents.

Table 6: Answers for Part 3.2

$I_{R1}$	
$I_{R2}$	
$I_{R3}$	
$I_{Total}$	

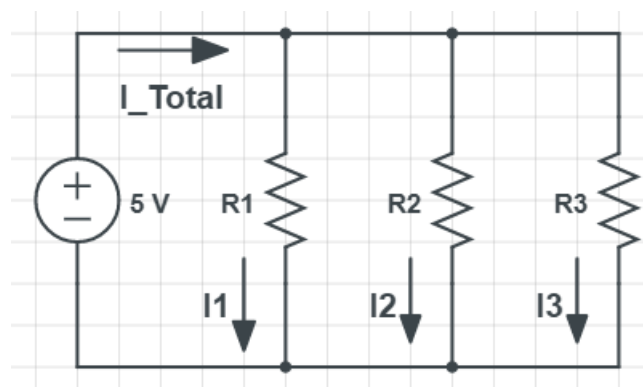


Figure 6

- What conclusions can be made from these results?

### Part 3.3

- Connect the circuit in Fig. 7. Adjust the voltage source to a value of 5 volts (with the circuit connected). Using the voltmeter, measure the voltage across each resistor. Record in Table 7. Add the voltage drops together and record.
- What conclusions can be made from these results?

Table 7: Answers for Part 3.3

$V_1$	
$V_2$	
$V_3$	


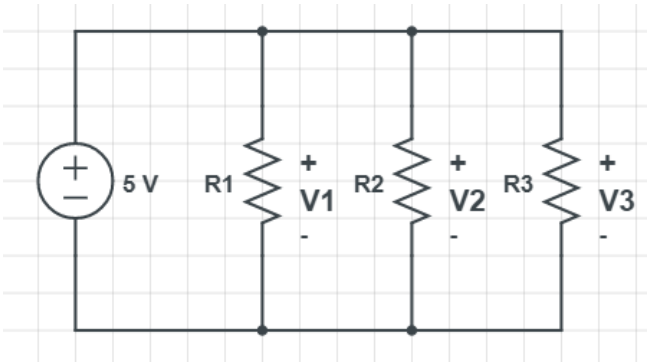



Figure 7

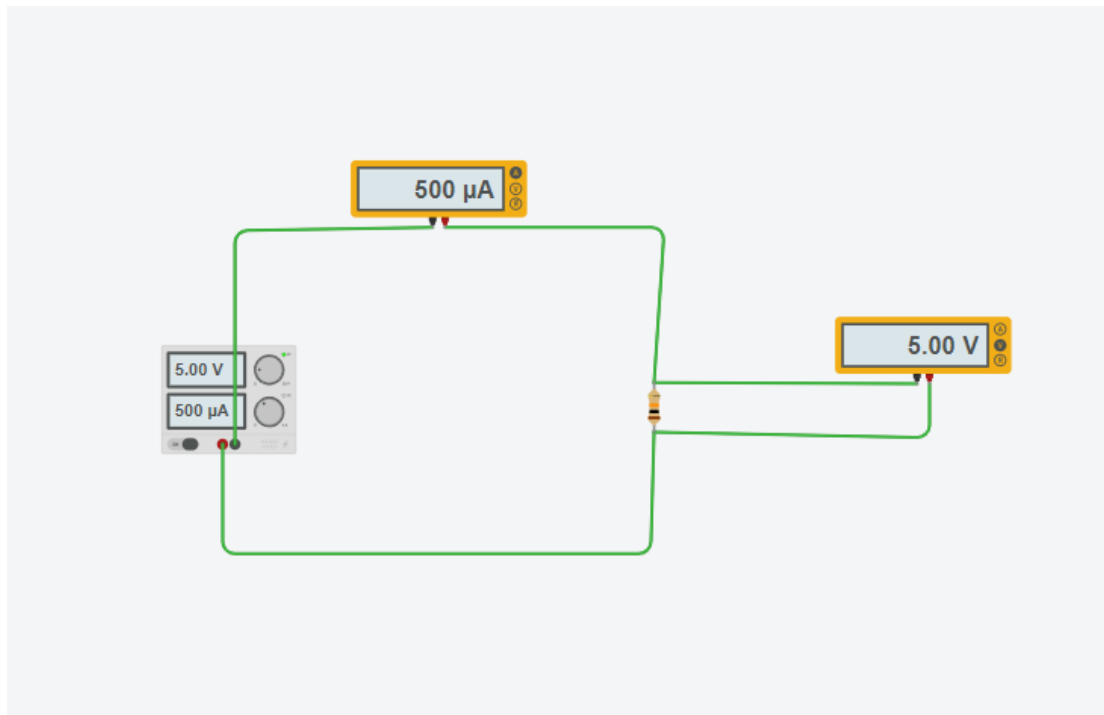


Part 1:




Part 2.1:

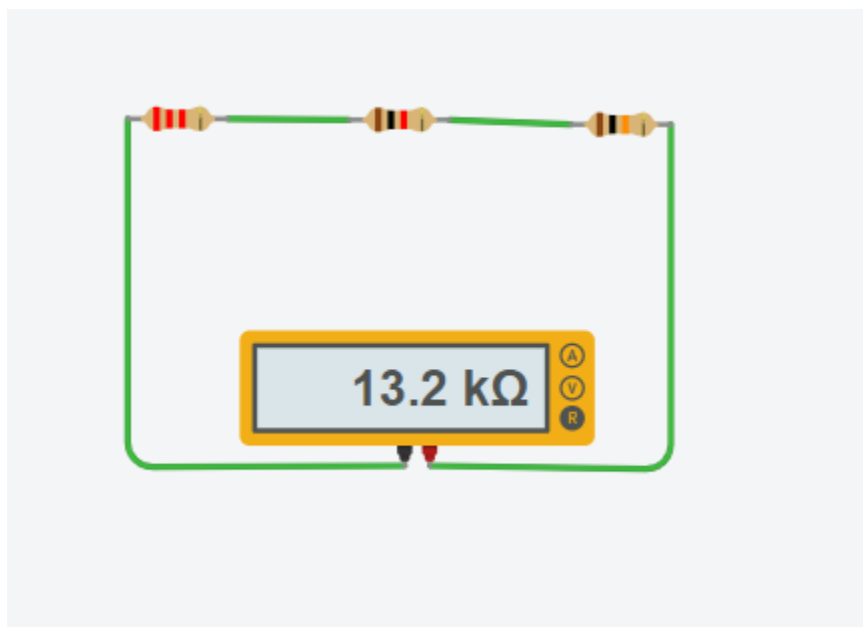


Part 2.2:

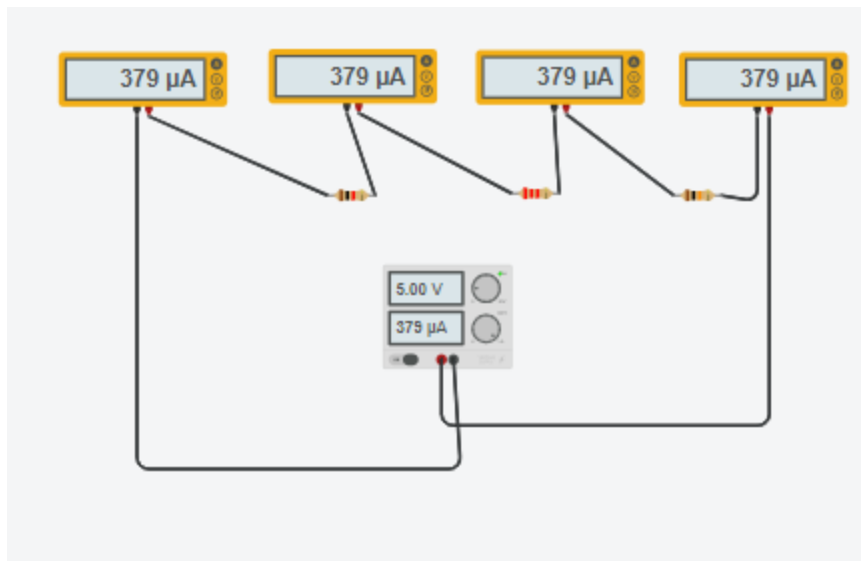


Part 2.3:

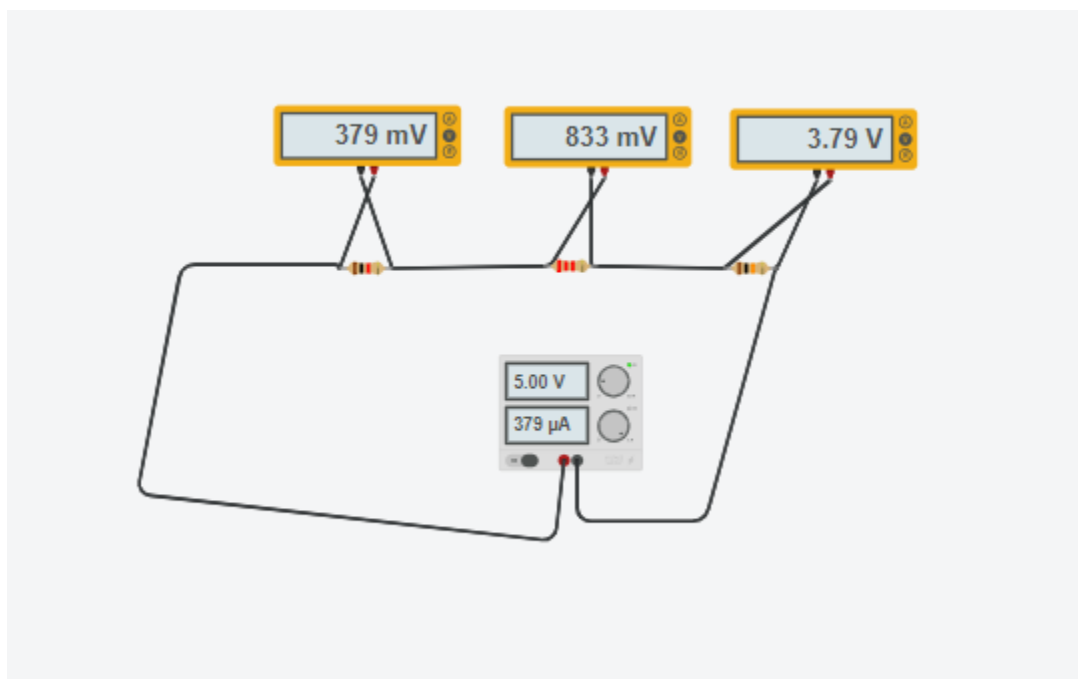

Part 3.1:

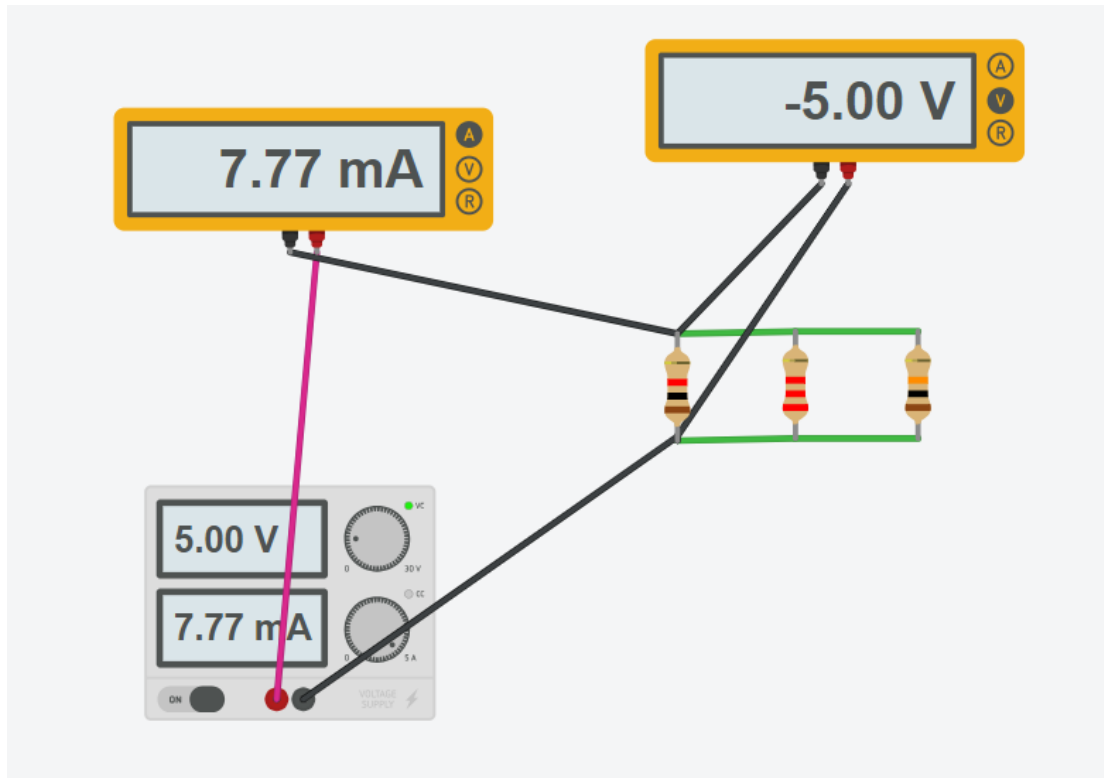

Part 3.2:

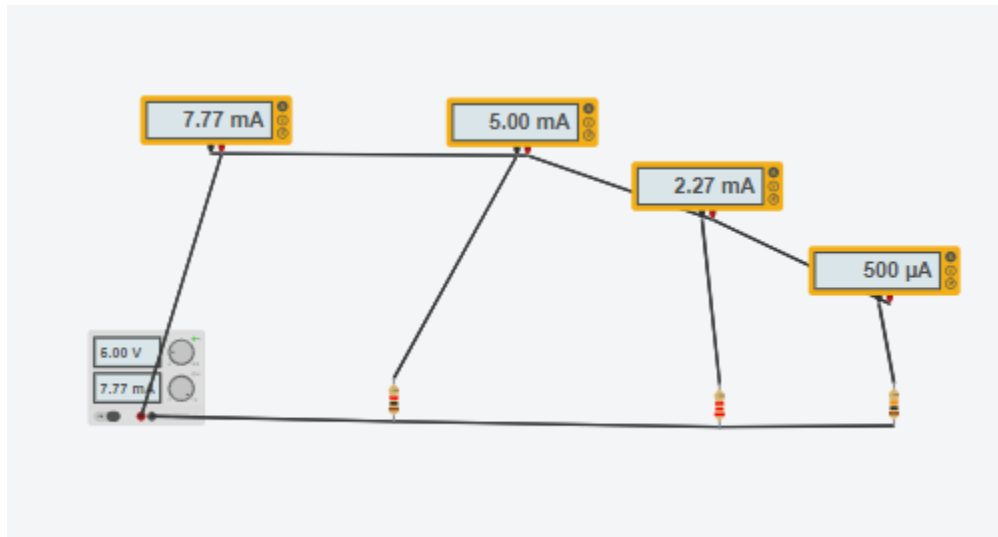

Part 3.3:

